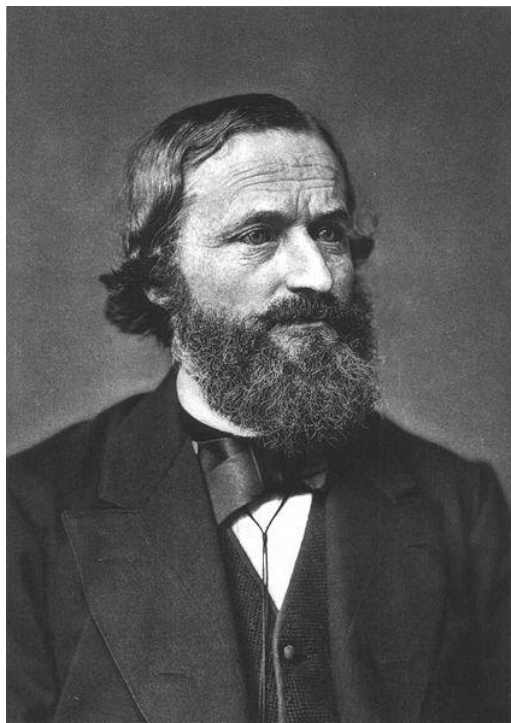


**PENNSYLVANIA SCIENCE OLYMPIAD
STATE FINALS 2008**

CIRCUIT LAB C DIVISION

APRIL 25, 2008



SCHOOL NAME _____

SCHOOL CODE _____


INSTRUCTIONS

1. Turn in all exam materials at the end of this event. *Missing exam materials will result in immediate disqualification of the team in question.* There is an exam packet and a blank answer sheet.
2. You may separate the exam pages. Re-staple them as you submit your materials to the supervisor. Keep the answer sheet separate.
3. *Only* the answers provided on the answer page will be considered. Do not write outside the designated spaces for each answer. Write LEGIBLY. Answers that can't be read can't be correct. Include units where applicable.
4. Write your school name and school code in the appropriate locations on the answer sheet as well as on the title page. Indicate the names of the participants at the bottom of the answer sheet. Write LEGIBLY.
5. Point values for each question are in parentheses. Tiebreaker questions are identified with a (T#) where the number indicates the sequence of consultation. In the event of a tie, the supervisor will first look at T1, then T2, etc. until the tie is broken. *Tiebreaker questions count toward the overall grade, and are only used as tiebreakers in the event of a tie.*
6. When the time is up, *the time is up*. Continuing to write after the time is up risks immediate disqualification.
7. Mocking, nonsensical, and/or inappropriate answers WILL RESULT IN DISQUALIFICATION.
8. Who is the gentleman pictured on the cover page, and what does he have to do with this event? Put your answer in the bonus box on the *back* of the answer sheet for 3 bonus points.
9. NON-PROGRAMMABLE CALCULATORS ONLY. DON'T ASK, THE ANSWER IS NO.
10. Use this table for the resistance of color-coded resistors.

COLOR	1 st stripe 1 st digit	2 nd stripe 2 nd digit	3 rd stripe multiplier
Black	0	0	X 1
Brown	1	1	X 10
Red	2	2	X 100
Orange	3	3	X 1000
Yellow	4	4	X 10000
Green	5	5	X 100000
Blue	6	6	X 1000000
Violet	7	7	
Grey	8	8	
White	9	9	

SECTION 1

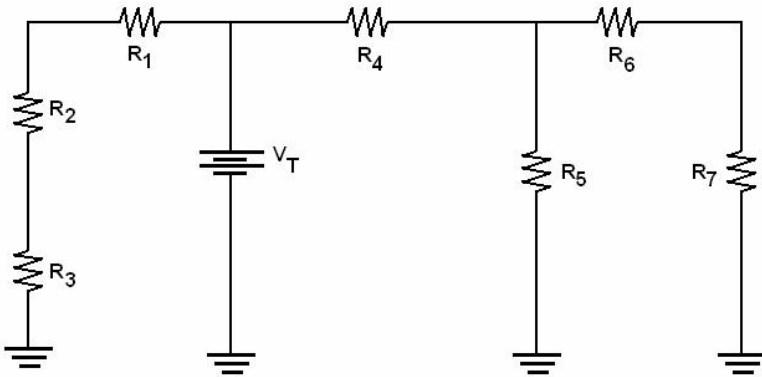
The schematic diagram below shows a circuit consisting of 7 color-coded resistors and an ideal voltage source ($V_T = 24$ volts). You may ignore the tolerance values (that is, the three stripes indicate the *actual* resistance). The 1st three colored stripes on each resistor are listed in the table.



R_1	green green black
R_2	brown grey black
R_3	brown black black
R_4	violet green black
R_5	brown black brown
R_6	brown green black
R_7	red red black

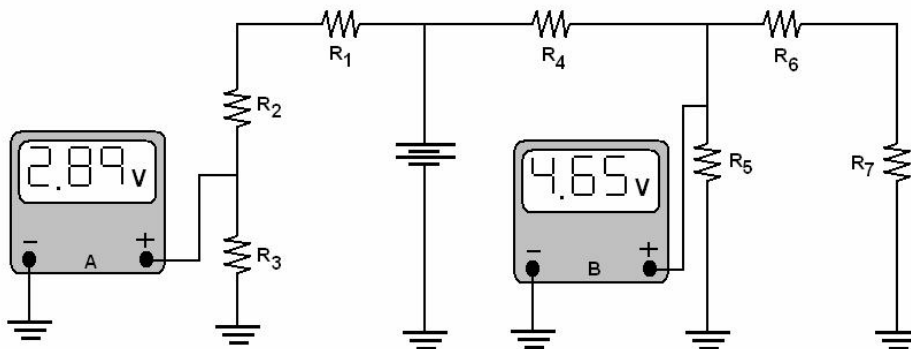- (21) 1. List the resistance of each resistor and solve for the theoretical current and voltage drop for each resistor in the circuit.
- (3) 2. What is the power dissipated by R_5 ?
- (3) 3. How much energy is dissipated by R_3 over 5.00 seconds?


Now the circuit is constructed, and ideal voltmeters are used to measure the voltage drops across R_3 and R_5 as shown below.



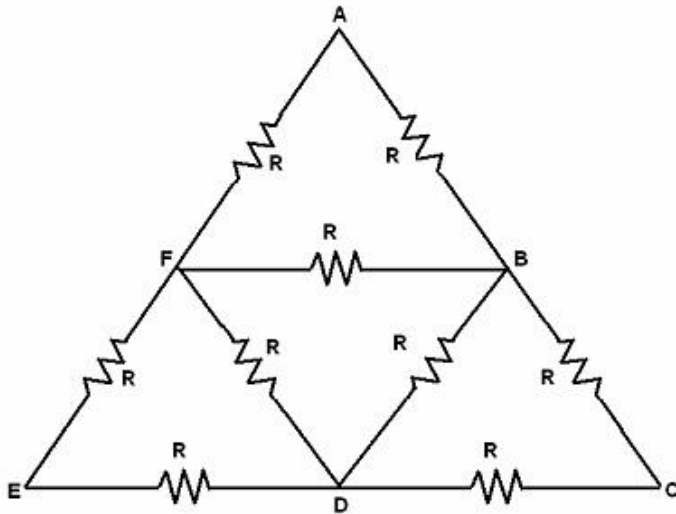
- (6) 4. (T6) The voltmeter readings indicate a problem in the circuit. Which resistor is the problem, and what is the nature of the problem?
- (3) 5. If R_2 was open-circuited, what would the voltmeter across R_3 display?
- (3) 6. If R_2 was short-circuited, what would the voltmeter across R_3 display?

SECTION 2

The circuit shown below consists of 9 identical ideal resistors, each with a resistance of $10\ \Omega$. Use this diagram for numbers 1-4.



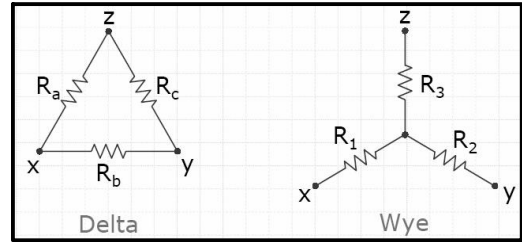HINT: Use the transformation equations shown below.



Delta-to-wye transformation equations





$$R_1 = \left(\frac{R_a R_b}{R_a + R_b + R_c} \right)$$

$$R_2 = \left(\frac{R_b R_c}{R_a + R_b + R_c} \right)$$

$$R_3 = \left(\frac{R_c R_a}{R_a + R_b + R_c} \right)$$

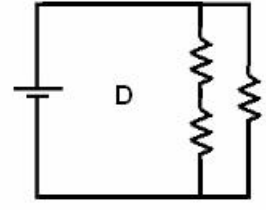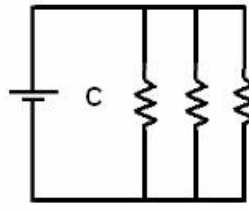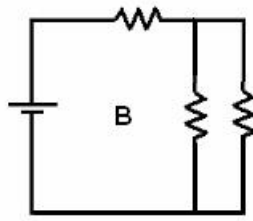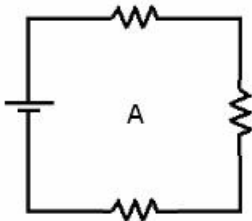- (3) 1. What is the resistance across terminals A and F?
- (3) 2. What is the resistance across terminals F and D?
- (3) 3. What is the resistance across terminals F and B?
- (3) 4. (T7) What is the resistance across terminals A and D?


The circuits shown below consist of three identical resistors (each with resistance R) and a battery (voltage V) with internal resistance $\frac{R}{3}$. Use these diagrams for numbers 5-14. Descending order means greatest first.



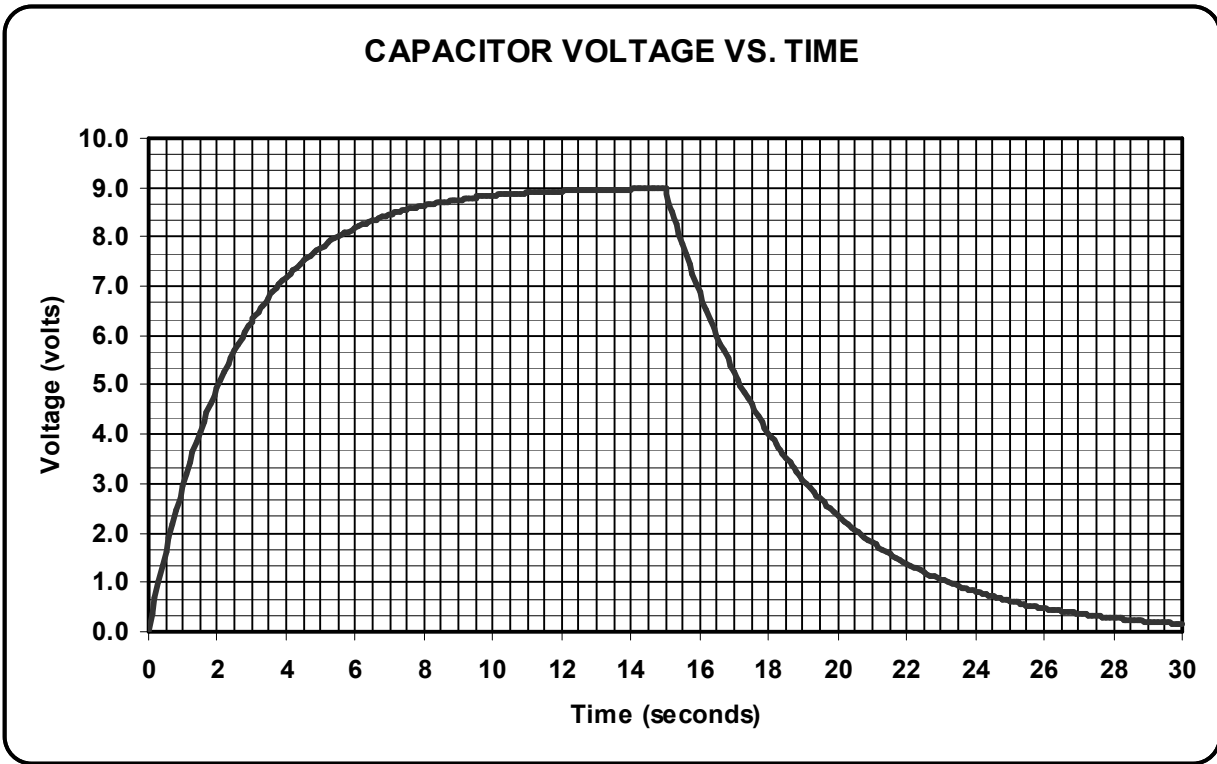
- (4) 5. Rank the circuits in descending order in terms of the equivalent resistance of the circuit.
- (2) 6. What is the equivalent resistance (including the battery) of circuit C in terms of R ?
- (4) 7. Rank the circuits in descending order in terms of the total current produced by the battery.
- (2) 8. What is the total current produced by the battery in circuit B, in terms of V and R ?
- (4) 9. Rank the circuits in descending order in terms of the power supplied by the battery.
- (2) 10. What is the power supplied by the battery in circuit D, in terms of V and R ?
- (4) 11. (T5) Rank the circuits in descending order in terms of the terminal voltage available to the circuit.
- (2) 12. What is the terminal voltage in circuit A, in terms of V ?
- (4) 13. Rank the circuits in descending order in terms of the voltage drop across the battery.
- (2) 14. What is the voltage drop across the battery in circuit B, in terms of V ?

SECTION 3

The circuit shown schematically at below right contains an ideal battery, two ideal resistors, and an ideal capacitor ($C = 250 \mu\text{F}$). The switch is closed at time $t = 0$, and the voltage across the capacitor is recorded as a function of time, producing the graph shown below.




- (2) 1. What is the voltage of the battery?
- (3) 2. What is the time constant for this circuit when the switch is closed?
- (3) 3. What is the time constant for this circuit when the switch is open?
- (3) 4. What is the resistance of resistor R_1 ?
- (3) 5. What is the resistance of resistor R_2 ?
- (3) 6. What is the voltage across resistor R_1 at $t = 2.0$ seconds?
- (3) 7. What is the voltage across resistor R_2 at $t = 2.0$ seconds?
- (3) 8. What is the total current produced by the battery at $t = 0$?
- (3) 9. What is the current through resistor R_1 at $t = 5.0$ seconds?
- (3) 10. What is the charge on the capacitor at $t = 15$ seconds?
- (3) 11. When is the switch opened?
- (6) 12. (T4) Sketch the graph (on the answer sheet) of the total current in the circuit as a function of time.

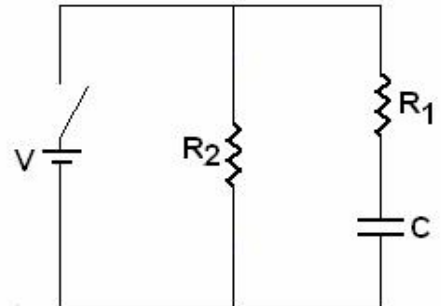

SECTION 4

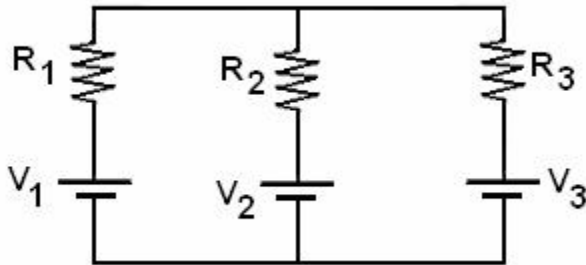
- (15) 1. (T2) The circuit shown below has three ideal voltage sources and three resistors arranged as shown. Solve for the current and voltage drop across each of the resistors, and include the direction of conventional current (up or down) through each resistor. The resistances R_1 , R_2 , and R_3 and voltages V_1 , V_2 , and V_3 are listed in the table.



VOLTAGES, V	
V_1	12
V_2	6
V_3	9

RESISTANCES, Ω	
R_1	5
R_2	10
R_3	20

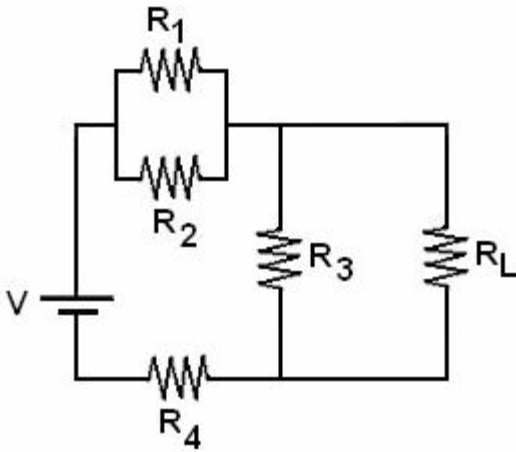Find the Thevenin equivalent circuit from the perspective of the load resistor R_L .



V	110	volts
R_1	16	ohms
R_2	24	ohms
R_3	50	ohms
R_4	33	ohms

- (4) 2. What is the value of V_{TH} ?
- (4) 3. (T3) What is the value of R_{TH} ?
- (4) 4. Sketch the Thevenin equivalent circuit from the perspective of R_L on the answer sheet.

SECTION 5

List the units *in base SI* for each of the following quantities. For example, Force would be recorded as $\frac{\text{kg m}}{\text{s}^2}$.

- (2) 1. Resistance
- (2) 2. Power
- (2) 3. Potential difference
- (2) 4. Charge
- (2) 5. Energy
- (2) 6. Capacitance
- (2) 7. Current
- (2) 8. Electric field strength
- (2) 9. Conductance
- (2) 10. Electrostatic force

(10) 11. (T1) You have a circuit consisting of six identical light bulbs wired to a battery. You are unable to see the wiring, but each light bulb is capable of being unscrewed from its housing. When each bulb is unscrewed, it is no longer part of the circuit. The experimental results when each bulb is *separately* unscrewed from its housing are shown in the table below.

CONDITION	EXPERIMENTAL OBSERVATIONS
All bulbs functional	Bulb 1 is brightest; bulb 3 dimmer; bulbs 5 and 6 equal brightness and dimmer than 3; bulbs 2 and 4 equal brightness, but dimmer than 5 and 6
bulb 1 removed	All bulbs dark
bulb 2 removed	Bulbs 1 and 3 equally bright; bulb 4 is dark; bulbs 5 and 6 equally bright but dimmer than 1 and 3
bulb 3 removed	Bulbs 1, 2, and 4 are equally bright; bulbs 5 and 6 are equally bright and dimmer than the others
bulb 4 removed	Bulbs 1 and 3 equally bright; bulb 2 is dark; bulbs 5 and 6 equally bright but dimmer than 1 and 3
bulb 5 removed	Bulbs 1 and 6 equally bright; bulb 3 dimmer; bulbs 2 and 4 equally bright but dimmer than 3
bulb 6 removed	Bulbs 1 and 5 equally bright; bulb 3 dimmer; bulbs 2 and 4 equally bright but dimmer than 3

On the back of the answer sheet, indicate the wiring of the circuit by drawing in the proper connections.